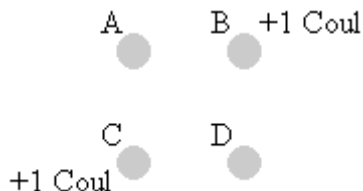


Electricity Review (Take at Home) Test
Planet Holloway Physics**Multiple Choice**

Identify the choice that best completes the statement or answers the question.

- _____ 1. Four charges are at the corners of a square, with B and C on opposite corners. Charges A and D, on the other two corners, have equal charge, while both B and C have a charge of $+1.0\text{ C}$. What is the charge on A so that the force on B is zero?




- a. -1.0 C
b. -0.50 C
c. -0.35 C
d. -0.71 C
e. -1.42 C
- _____ 2. Charge A and charge B are 3.00 m apart, and charge A is $+2.00\text{ C}$ and charge B is $+3.00\text{ C}$. Charge C is located between them at a certain point and the force on charge C is zero. How far from charge A is charge C?
a. 0.555 m
b. 0.667 m
c. 1.35 m
d. 1.50 m
e. 1.80 m
- _____ 3. A $6.0\text{ }\mu\text{C}$ charge is placed at the origin and a second charge is placed on the x-axis at $x = 0.30\text{ m}$. If the resulting force on the second charge is 5.4 N in the positive x-direction, what is the value of its charge?
a. $9.0\text{ }\mu\text{C}$
b. 9.0 nC
c. $-9.0\text{ }\mu\text{C}$
d. -9.0 nC
e. 90 nC
- _____ 4. Two point charges each have a value of 30.0 mC and are separated by a distance of 4.00 cm . What is the electric field midway between the two charges? ($k_e = 8.99 \times 10^9\text{ N}\cdot\text{m}^2/\text{C}^2$)
a. $40.5 \times 10^7\text{ N/C}$
b. $20.3 \times 10^7\text{ N/C}$
c. $10.1 \times 10^7\text{ N/C}$
d. $5.1 \times 10^7\text{ N/C}$
e. zero


- _____ 5. Two point charges are separated by 10.0 cm and have charges of $+2.00\mu\text{C}$ and $-2.00\mu\text{C}$, respectively. What is the electric field at a point midway between the two charges? ($k_e = 8.99 \times 10^9 \text{ N}\cdot\text{m}^2/\text{C}^2$)
- $28.8 \times 10^6 \text{ N/C}$
 - $14.4 \times 10^6 \text{ N/C}$
 - $7.19 \times 10^6 \text{ N/C}$
 - $3.59 \times 10^6 \text{ N/C}$
 - zero
- _____ 6. An electron (charge $-1.6 \times 10^{-19} \text{ C}$) moves on a path perpendicular to the direction of a uniform electric field of strength 3.0 N/C. How much work is done on the electron as it moves 15 cm?
- $4.8 \times 10^{-20} \text{ J}$
 - $-4.8 \times 10^{-20} \text{ J}$
 - $1.6 \times 10^{-20} \text{ J}$
 - $-1.6 \times 10^{-20} \text{ J}$
 - zero
- _____ 7. A proton ($+1.6 \times 10^{-19} \text{ C}$) moves 10 cm on a path in the direction of a uniform electric field of strength 3.0 N/C. How much work is done on the proton by the electrical field?
- $4.8 \times 10^{-20} \text{ J}$
 - $-4.8 \times 10^{-20} \text{ J}$
 - $1.6 \times 10^{-20} \text{ J}$
 - $-1.6 \times 10^{-20} \text{ J}$
 - zero
- _____ 8. A uniform electric field, with a magnitude of 600 N/C, is directed parallel to the positive x -axis. If the potential at $x = 3.0 \text{ m}$ is 1 000 V, what is the change in potential energy of a proton as it moves from $x = 3.0 \text{ m}$ to $x = 1.0 \text{ m}$? ($q_p = 1.6 \times 10^{-19} \text{ C}$)
- $8.0 \times 10^{-17} \text{ J}$
 - $1.9 \times 10^{-16} \text{ J}$
 - $0.80 \times 10^{-21} \text{ J}$
 - 500 J
 - $2.2 \times 10^{-15} \text{ J}$
- _____ 9. In which case does an electric field do positive work on a charged particle?
- a negative charge moves opposite to the direction of the electric field.
 - a positive charge is moved to a point of higher potential energy.
 - a positive charge completes one circular path around a stationary positive charge.
 - a positive charge completes one elliptical path around a stationary positive charge.
 - a negative charge moves in the direction of the electric field.
- _____ 10. If the distance between two negative point charges is increased by a factor of three, the resultant potential energy is what factor times the initial potential energy?
- 3.0
 - 9.0
 - 1/3
 - 1/9
 - 1

- _____ 11. Find the electrical potential at 0.15 m from a point charge of $6.0\ \mu\text{C}$. ($k_e = 8.99 \times 10^9\ \text{N}\cdot\text{m}^2/\text{C}^2$)
- $5.4 \times 10^4\ \text{V}$
 - $3.6 \times 10^5\ \text{V}$
 - $2.4 \times 10^6\ \text{V}$
 - $1.2 \times 10^7\ \text{V}$
 - $1.8 \times 10^7\ \text{V}$
- _____ 12. Two point charges of values $+3.4$ and $+6.6\ \mu\text{C}$, respectively, are separated by 0.20 m. What is the potential energy of this 2-charge system? ($k_e = 8.99 \times 10^9\ \text{N}\cdot\text{m}^2/\text{C}^2$)
- $+0.34\ \text{J}$
 - $-0.75\ \text{J}$
 - $+1.0\ \text{J}$
 - $-3.4\ \text{J}$
 - $+0.75\ \text{J}$
- _____ 13. Doubling the voltage across a parallel plate capacitor does not double which of the following?
- the charge
 - the electric field between the plates
 - the energy stored
 - the electric force on the plates
 - both a and b
- _____ 14. Three capacitors of 1.0, 1.5, and $2.0\ \mu\text{F}$ are connected in series. Find the combined capacitance.
- $4.5\ \mu\text{F}$
 - $4.0\ \mu\text{F}$
 - $2.2\ \mu\text{F}$
 - $0.46\ \mu\text{F}$
 - $0.24\ \mu\text{F}$
- _____ 15. If three $4.0\text{-}\mu\text{F}$ capacitors are connected in parallel, what is the combined capacitance?
- $12\ \mu\text{F}$
 - $0.75\ \mu\text{F}$
 - $8.0\ \mu\text{F}$
 - $0.46\ \mu\text{F}$
 - $5.5\ \mu\text{F}$
- _____ 16. Two capacitors with capacitances of 1.5 and $0.25\ \mu\text{F}$, respectively, are connected in parallel. The system is connected to a 50-V battery. What charge accumulates on the $1.5\text{-}\mu\text{F}$ capacitor?
- $100\ \mu\text{C}$
 - $75\ \mu\text{C}$
 - $50\ \mu\text{C}$
 - $33\ \mu\text{C}$
 - $25\ \mu\text{C}$

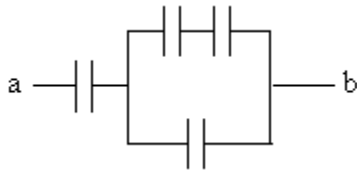- _____ 17. What is the equivalent capacitance between points a and b? All capacitors are $1.0\ \mu\text{F}$.




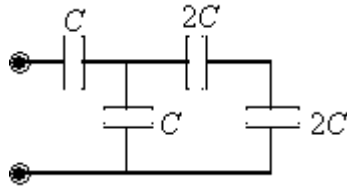- a. $4.0\ \mu\text{F}$
 - b. $1.7\ \mu\text{F}$
 - c. $0.60\ \mu\text{F}$
 - d. $0.25\ \mu\text{F}$
 - e. $0.50\ \mu\text{F}$
- _____ 18. If $C = 36\ \mu\text{F}$, determine the equivalent capacitance for the combination shown.



- a. $36\ \mu\text{F}$
 - b. $32\ \mu\text{F}$
 - c. $28\ \mu\text{F}$
 - d. $24\ \mu\text{F}$
 - e. $20\ \mu\text{F}$
- _____ 19. The size of the electric current in an electrical conductor is a function of which of the following?
- a. velocity of charge carriers
 - b. conductor cross sectional area
 - c. density of charge carriers
 - d. conductor length
 - e. All of the above choices are valid.
- _____ 20. You measure a 25.0-V potential difference across a $5.00\text{-}\Omega$ resistor. What is the current flowing through it?
- a. $125\ \text{A}$
 - b. $5.00\ \text{A}$
 - c. $4.00\ \text{A}$
 - d. $1.00\ \text{A}$
 - e. $0.125\ \text{A}$
- _____ 21. A 60-W light bulb is in a socket supplied with $120\ \text{V}$. What is the current in the bulb?
- a. $0.50\ \text{A}$
 - b. $2.0\ \text{A}$
 - c. $60\ \text{A}$
 - d. $7\ 200\ \text{A}$
 - e. $10\ 000\ \text{A}$

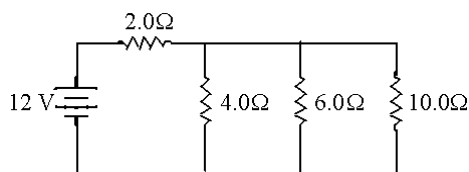- _____ 22. If a lamp has resistance of $120\ \Omega$ when it operates at $100\ \text{W}$, what is the applied voltage?
- $110\ \text{V}$
 - $120\ \text{V}$
 - $125\ \text{V}$
 - $220\ \text{V}$
 - $280\ \text{V}$
- _____ 23. A light bulb has resistance of $240\ \Omega$ when operating at $120\ \text{V}$. Find the current in the light bulb.
- $2.0\ \text{A}$
 - $1.0\ \text{A}$
 - $0.50\ \text{A}$
 - $0.20\ \text{A}$
 - $0.30\ \text{A}$
- _____ 24. The internal resistances of an ideal voltmeter and an ideal ammeter are respectively (*ideal* meaning the behavior of the system is not changed when using the meter):
- zero and zero.
 - infinite and infinite.
 - zero and infinite.
 - infinite and zero.
 - Both resistances are finite and non-zero.
- _____ 25. Three resistors, with values of 2.0 , 4.0 and $8.0\ \Omega$, respectively, are connected in series. What is the overall resistance of this combination?
- $0.58\ \Omega$
 - $1.1\ \Omega$
 - $7.0\ \Omega$
 - $14.0\ \Omega$
 - $19.0\ \Omega$
- _____ 26. Three resistors connected in parallel have individual values of 4.0 , 6.0 and $10.0\ \Omega$, respectively. If this combination is connected in series with a 12-V battery and a $2.0\text{-}\Omega$ resistor, what is the current in the $10\text{-}\Omega$ resistor?




- $0.59\ \text{A}$
- $1.0\ \text{A}$
- $11\ \text{A}$
- $16\ \text{A}$
- $23\ \text{A}$


Name: _____

ID: A

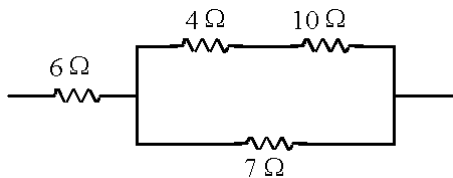- _____ 27. Two resistors of values 6.0 and $12.0\ \Omega$ are connected in parallel. This combination in turn is hooked in series with a $4.0\text{-}\Omega$ resistor. What is the overall resistance of this combination?
- a. $0.50\ \Omega$
 - b. $2.0\ \Omega$
 - c. $8.0\ \Omega$
 - d. $22.0\ \Omega$
 - e. $34.0\ \Omega$
- _____ 28. Resistors of values $6.0\ \Omega$, $4.0\ \Omega$, $10.0\ \Omega$ and $7.0\ \Omega$ are combined as shown. What is the equivalent resistance for this combination?




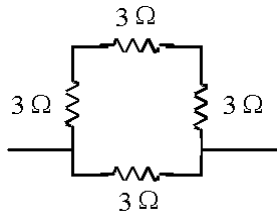- a. $2.3\ \Omega$
 - b. $3.0\ \Omega$
 - c. $10.7\ \Omega$
 - d. $27\ \Omega$
 - e. $30\ \Omega$
- _____ 29. What is the equivalent resistance for these $3.00\text{-}\Omega$ resistors?




- a. $1.33\ \Omega$
- b. $2.25\ \Omega$
- c. $3.00\ \Omega$
- d. $7.50\ \Omega$
- e. $9.00\ \Omega$

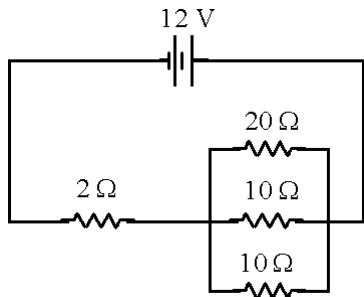
- _____ 30. How much current is flowing in one of the $10\text{-}\Omega$ resistors?



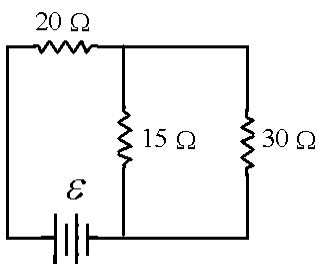- a. 0.8 A
 b. 2.0 A
 c. 1.6 A
 d. 2.4 A
 e. 2.8 A
- _____ 31. If $\mathcal{E} = 9.0\text{ V}$, what is the current in the $15\text{-}\Omega$ resistor?



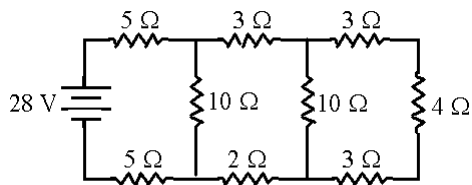
- a. 0.20 A
 b. 0.30 A
 c. 0.10 A
 d. 0.26 A
 e. 0.15 A
- _____ 32. Consider the circuit shown in the figure. What power is dissipated by the entire circuit?




- a. 14 W
 b. 28 W
 c. 52 W
 d. 112 W
 e. 169 W

- _____ 33. Resistors of values $8.0\ \Omega$, $12.0\ \Omega$, and $24.0\ \Omega$ are connected in parallel across a fresh battery. Which resistor dissipates the greatest power?
- the $8.0\text{-}\Omega$ resistor
 - the $12.0\text{-}\Omega$ resistor
 - the $24.0\text{-}\Omega$ resistor
 - All dissipate the same power when in series.
 - The answer depends on the internal resistance of the battery.

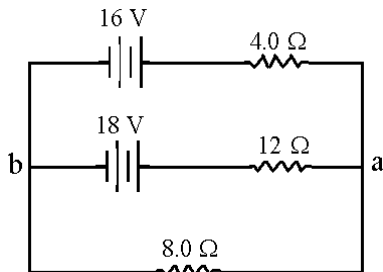- _____ 34. What is the current through the $8\text{-}\Omega$ resistor?




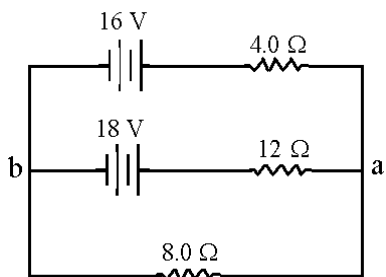- 1.0 A
 - 0.50 A
 - 1.5 A
 - 2.0 A
 - 2.5 A
- _____ 35. What is the potential difference between points a and b?




- 6 V
 - 8 V
 - 12 V
 - 24 V
 - 27 V
- _____ 36. In a circuit, a current of 2.0 A is drawn from a battery. The current then divides and passes through two resistors in parallel. One of the resistors has a value of $64\ \Omega$ and the current through it is 0.40 A. What is the value of the other resistor?
- $8.0\ \Omega$
 - $16\ \Omega$
 - $24\ \Omega$
 - $32\ \Omega$
 - $40\ \Omega$

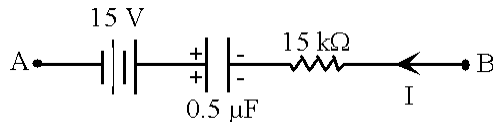
- _____ 37. In the circuit segment shown if $I = 7 \text{ mA}$ and $Q = 50 \mu\text{C}$, what is the potential difference, $V_A - V_B$?



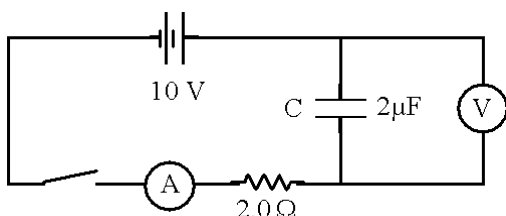- a. -40 V
 b. $+40 \text{ V}$
 c. $+20 \text{ V}$
 d. -20 V
 e. -15 V
- _____ 38. A 10-V-emf battery is connected in series with the following: a $2\text{-}\mu\text{F}$ capacitor, a $2\text{-}\Omega$ resistor, an ammeter, and a switch, initially open; a voltmeter is connected in parallel across the capacitor. At the instant the switch is closed, what are the current and capacitor voltage readings, respectively?



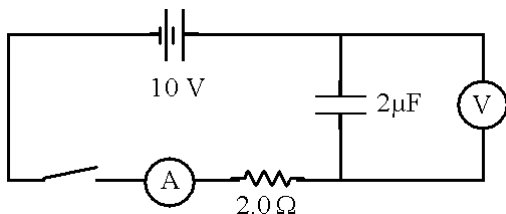- a. zero A, 10 V
 b. zero A, zero V
 c. 5 A, zero V
 d. 5 A, 10 V
 e. 20 A, 10 V
- _____ 39. A 10-V-emf battery is connected in series with the following: a $2\text{-}\mu\text{F}$ capacitor, a $2\text{-}\Omega$ resistor, an ammeter, and a switch, initially open; a voltmeter is connected in parallel across the capacitor. After the switch has been closed for a relatively long period (several seconds, say), what are the current and capacitor voltage readings, respectively?



- a. zero A, 10 V
 b. zero A, zero V
 c. 5 A, zero V
 d. 5 A, 10 V
 e. 20 A, 10 V

Name: _____

ID: A

- _____ 40. A hair dryer draws 1 200 W, a curling iron draws 800 W, and an electric light fixture draws 500 W. If all three of these appliances are operating in parallel on a 120-V circuit, what is the total current drawn?
- a. 19.4 A
 - b. 20.8 A
 - c. 25.4 A
 - d. 36.7 A
 - e. 63.8 A